

The potentiometer in the circuit is adjusted until the power dissipated in it is 1.5 W. Find the value of R_P that satisfies this condition.

$R_P =$ _____

