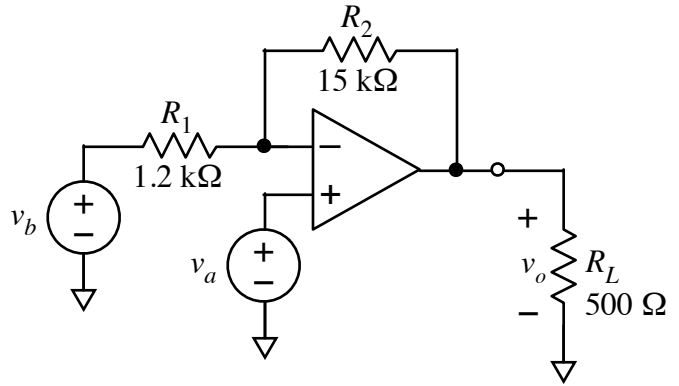


The op amp in the circuit at right is ideal.



- a. Calculate the expression for the output voltage as a function of the two input voltages, v_a and v_b

$v_o =$ _____

- b. If $v_a = 1$ V and $v_b = 0.33$ V, what is the value of the output? $v_o =$ _____

- c. What is the output if $v_a = 1$ V and $v_b = 0.33$ V and $R_L = 2$ kΩ? $v_o =$ _____

- d. What is the output if $v_a = 1$ V and $v_b = 0.33$ V and $R_L = 125$ Ω? $v_o =$ _____

- e. if $v_a = 1$ V and $v_b = 1.33$ V and $R_L = 500$ Ω, what is the total power being delivered by the input voltage sources and what is the power being delivered to the load? How do you account for the difference?

$P_{v_a} + P_{v_b} =$ _____; $P_{R_L} =$ _____