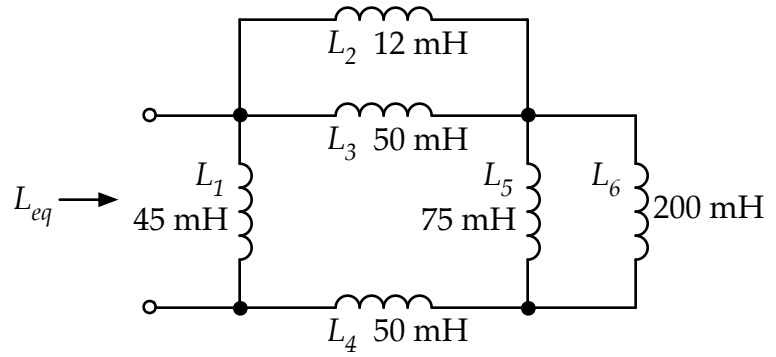


Find the equivalent inductance for the circuit shown below.



$L_{eq} =$  \_\_\_\_\_

If  $L_4$  is changed to a 0.5-H inductor, what is  $L_{eq}$ ?

$L_{eq} =$  \_\_\_\_\_