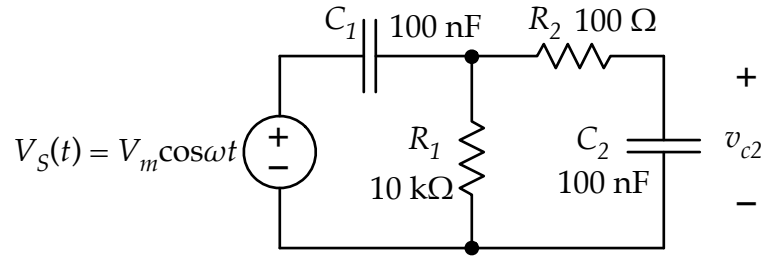


Use AC analysis to find the complex voltage for  $v_{C2}$  shown in the circuit at right for frequencies of  $\omega = 10^3$  rad/s,  $10^4$  rad/s, and  $10^5$  rad/s. The amplitude of the sinusoidal source is 10 V. Express the answers in magnitude/phase form.



$$\omega = 10^3 \text{ rad/s} : \tilde{V}_{C2} = \underline{\hspace{10cm}}$$

$$\omega = 10^4 \text{ rad/s} : \tilde{V}_{C2} = \underline{\hspace{10cm}}$$

$$\omega = 10^5 \text{ rad/s} : \tilde{V}_{C2} = \underline{\hspace{10cm}}$$