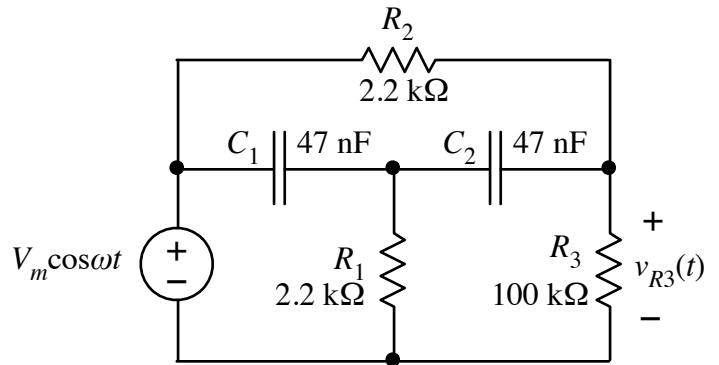


- a. For the circuit at right, use SPICE to plot the sinusoidal voltage across the resistor R_3 together with the source voltage. Include at least four periods of the sinusoid in the plot.

For the source $V_m = 5\text{ V}$ and $f = 1591\text{ Hz}$ ($\omega = 10^4\text{ rad/s}$.)

From the plots, determine the complex value of v_{R3} and its phase shift relative to the source.




Note that there will be a transient at the start of the simulation. Determine the amplitude and phase shift from the later periods of the plot, after the transient has disappeared.

$\tilde{v}_{R3} =$ _____

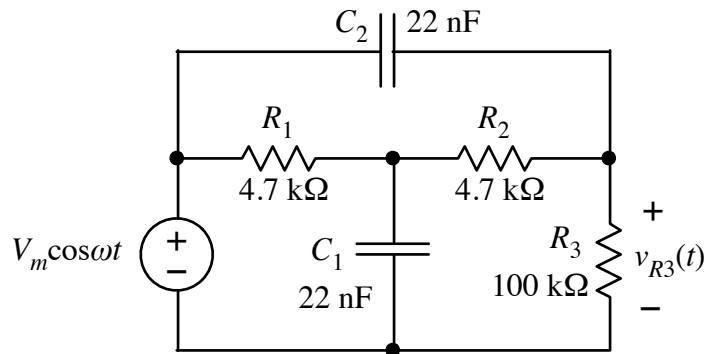- b. Repeat for the related circuit shown at right. The source amplitude and frequency are the same as in part a.

(Foreshadowing: These are known as “bridged- T ” RC circuits. They will appear again in EE 230.)



$\tilde{v}_{R3} =$ _____