

a) Design a passive first-order high-pass filter using resistors and a capacitor. The filter should have a corner frequency at  $f_c = 2.9$  kHz a high-frequency gain  $G_o = 0.6$ . Use component values that are available in your lab kits. Sketch a clean and legible circuit diagram with component values labeled. Below that, show your design calculations.

b) Confirm your design with a SPICE (PSPICE or LTSPICE ) frequency response simulation. In the simulation, use a frequency range of 10 Hz to 1 MHz. Plot the magnitude and phase of the output over this range.