

- a) Design an active first-order low-pass filter using resistors, a capacitor, and an op-amp. The filter should have a corner frequency at 4 kHz and low frequency gain of 12.
  
- b) Confirm your design with a SPICE frequency response simulation. In the simulation, use a frequency range of 10 Hz to 1 MHz. Plot the magnitude of the output over this range.