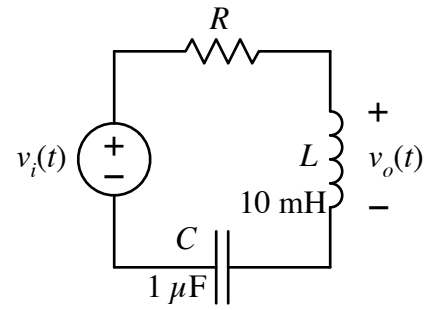


For the second-order circuit shown at right, calculate the transfer function (in symbols). What type of filter is it?

If $R = 300 \Omega$, what are f_o , Q_P , and G_o for the filter?

Repeat for $R = 50 \Omega$. What value of R is needed to make $Q_P = 0.707$ (maximally flat)?



$T(s) =$ _____

type: _____

$R = 300 \Omega$: $f_o =$ _____; $Q_P =$ _____; $G_o =$ _____

$R = 50 \Omega$: $f_o =$ _____; $Q_P =$ _____; $G_o =$ _____

R for $Q_P = 0.707$: _____