



Calculate the transfer function for the circuit shown above. (Use symbols, not numbers.)

$T(s) =$ _____

What type of filter is this? _____

Calculate ω_o , Q_P , and G_o for the filter.

$\omega_o =$ _____; $Q_P =$ _____; $G_o =$ _____