

Find the frequency-domain expression for the requested quantities in the two circuits shown below. The sources are not specified — include them in your answers as simply $V_i(s)$ or $I_i(s)$.

