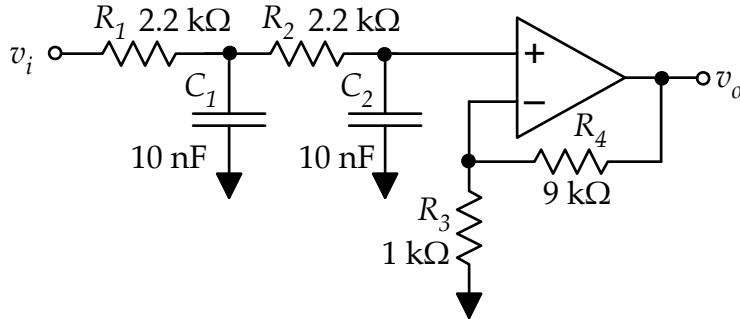


For the circuit shown below, calculate the transfer function. Express your answer in symbols (R , C , etc) rather than numbers. Assume that the op-amp is ideal.



From the transfer function, calculate the values for the pole frequencies (P_1 and P_2), ω_o , and Q_P . (These should be numbers, not symbols.)

Then calculate the 3-dB frequency (or frequencies).

$T(s) =$ _____

$P_1 =$ _____ . $P_2 =$ _____ .

$\omega_o =$ _____ . $Q_P =$ _____ .

$f_c =$ _____ . (Hz, not rad/s)