

Design an active bandpass filter with the following properties: lower corner frequency at 500 Hz, upper corner frequency at 10 kHz and passband gain of 26 dB.

Hint: This is a wide-band filter with low Q_P – think “cascading simpler op amp circuits”.

Confirm your design by generating magnitude and phase frequency response plots using SPICE.