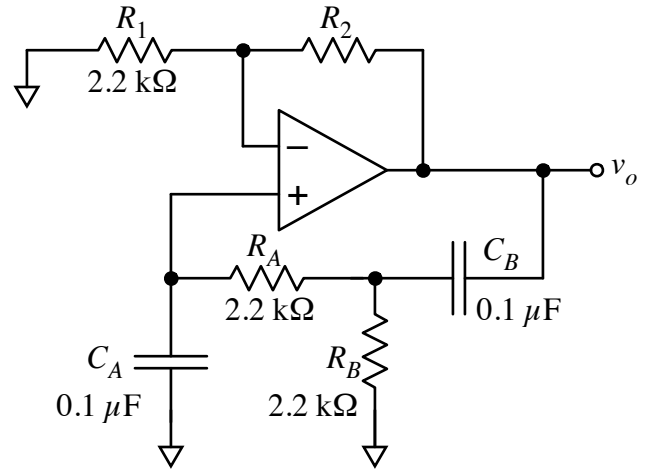


The oscillator circuit at right is a variation of the Wien-bridge circuit.

Determine the loop gain function for the circuit.

From the loop function, calculate the value for the oscillation frequency. Calculate the minimum of R_2 needed to ensure oscillation.



$L(s) =$ _____

$f_o =$ _____; $R_2(\text{min}) =$ _____

Use SPICE to simulate the operation of the circuit. Run the simulation twice — once with the gain at the exact minimum needed to start oscillation and then again with the gain 10% higher than the minimum, showing the increase in the amplitude and the resultant clipping that occurs.