

Find the current flowing in each of the resistors in the circuit below. For the diodes, use the on/off model. (Do not use the exact diode equation.)

$i_{R1} =$  \_\_\_\_\_

$i_{R2} =$  \_\_\_\_\_

$i_{R3} =$  \_\_\_\_\_

