

For the circuit shown at right, calculate i_{RC2} for $V_{BB} = 2$ V, and 5 V.
 Both BJTs have $\beta_F = 100$.

$V_{BB} = 2$ V, $i_{RC2} =$ _____

$V_{BB} = 5$ V, $i_{RC2} =$ _____

