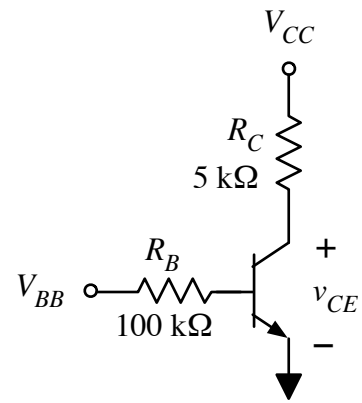


For the simple inverter circuit (NOT gate), use SPICE to perform the following simulations. For the transistor,  $\beta_F = 150$ . (It will be necessary to change that for the *nnp* model in SPICE. The default value in SPICE is 100.)



a. Find the DC values for  $i_C$  and  $v_{CE}$  for the following power supply combinations. Also, calculate the values by hand using the simplifying forward-active and saturation models for the BJT. You should use a *bias point* simulation for these DC calculations.

	$i_C$ (manual)	$i_C$ (SPICE)	$v_{CE}$ (manual)	$v_{CE}$ (SPICE)
$V_{BB} = 1.35\text{ V}$ $V_{CC} = 10\text{ V}$				
$V_{BB} = 1.35\text{ V}$ $V_{CC} = 5\text{ V}$				
$V_{BB} = 2.35\text{ V}$ $V_{CC} = 10\text{ V}$				
$V_{BB} = 2.35\text{ V}$ $V_{CC} = 20\text{ V}$				

b. With  $V_{CC} = 10\text{ V}$ , make a plot of the inverter characteristics ( $v_{CE}$  vs.  $V_{BB}$ ). This will require a DC sweep simulation with  $V_{BB}$  sweeping from 0 to 10 V. Use at 10 points per volt when setting up the simulation.

c. Change  $V_{BB}$  to a sinusoidal source (VSIN) with amplitude of 0.1 V, frequency of 1 kHz, and DC offset of 1.35 V. Do a transient simulation, plotting the  $v_{CE}$  and  $V_{BB}$  waveforms together on a single set of axes. Plot at least two full periods of the sinusoid. From the voltage traces, note the gain of the amplifier.