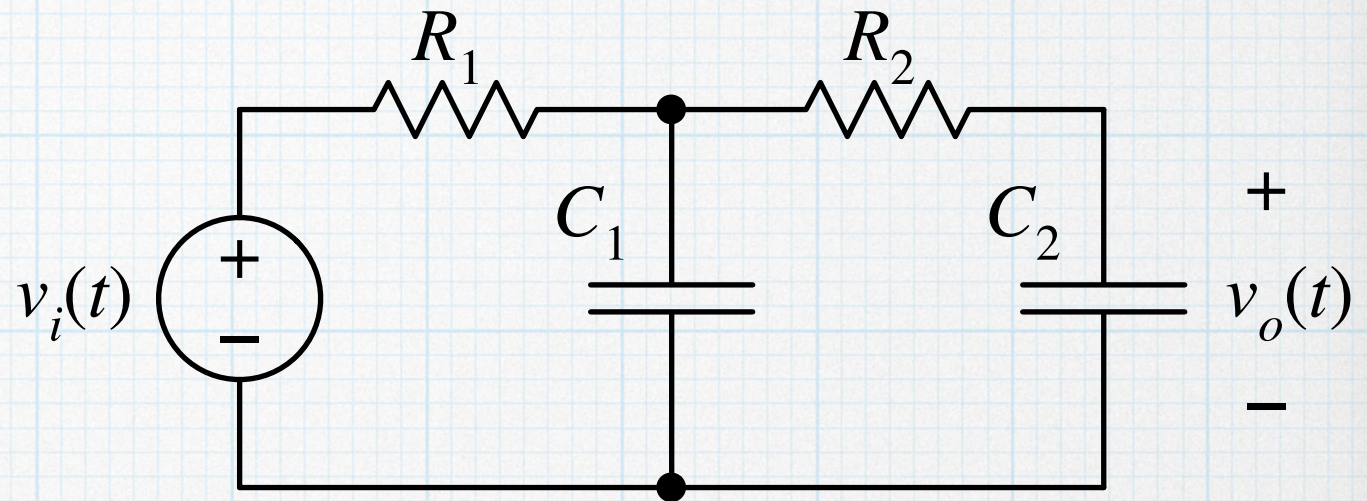


second-order ladder filters – some details

“Ladder”-type filter circuits, like the RC circuit shown at right, are quite common and easily implemented. They show up frequently (at least in homework problems and lab exercises) that it is worthwhile to develop a favorite technique for handling them.



We will use three methods — node voltage, mesh current, and “two voltage dividers” — to derive the transfer function. You can then use the method that best resonates with you. (Pardon the pun.) The details of the calculations are specific to this RC circuit, but the general approach will apply to ladder circuits with any combination of R 's, L 's, and C 's.

As always, before diving into a pile of math, it is a good idea to take a qualitative look at the circuit. We see that this particular circuit consists two RC low-pass sections (capacitors in shunt) connected together, so we expect the second-order response to also be low-pass. Without an inductor, there is no possibility for resonance, and the filter must be limited to $Q_P < 0.5$.

Node voltage (This is my preferred method.)

1. Start with two node-voltage equations, in terms of impedances.


$$\frac{V_i - V_x}{Z_{R1}} = \frac{V_x}{Z_{C1}} + \frac{V_x - V_o}{Z_{R2}}$$

$$\frac{V_x - V_o}{Z_{R2}} = \frac{V_o}{Z_{C2}}$$

2. Insert R 's and C 's.

$$\frac{V_i - V_x}{R_1} = sC_1 V_x + \frac{V_x - V_o}{R_2}$$

$$\frac{V_x - V_o}{R_2} = sC_2 V_o$$

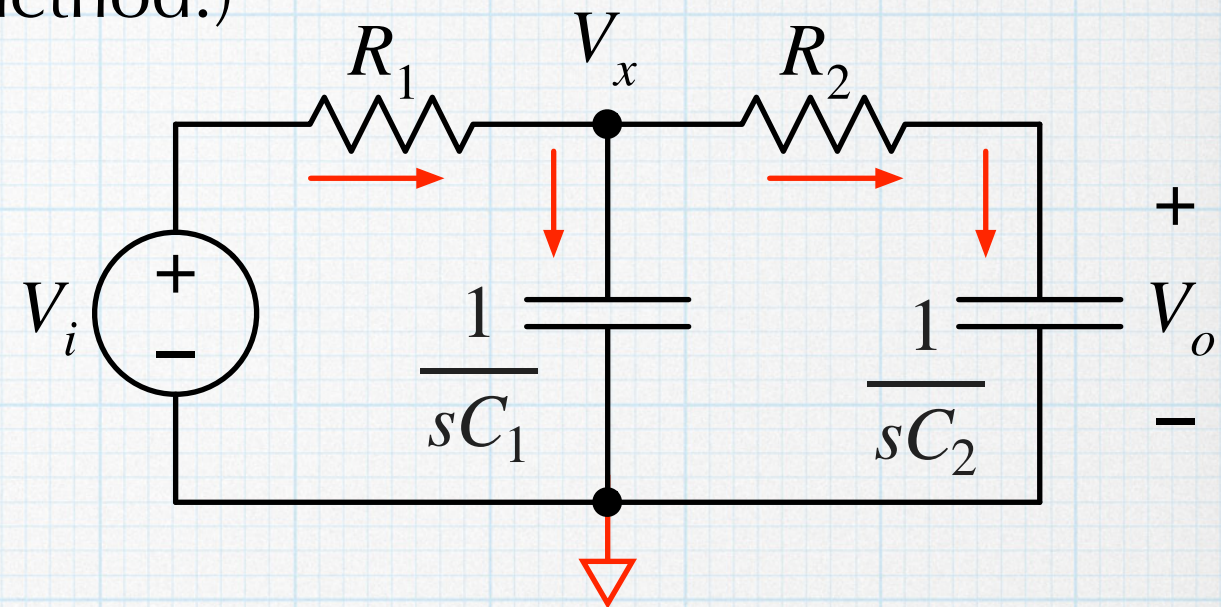

3. Re-arrange each equation.

$$V_i = \left[1 + \frac{R_1}{R_2} + sR_1C_1 \right] V_x - \frac{R_1}{R_2} V_o$$

$$V_x = [1 + sR_2C_2] V_o$$

4. Substitute V_x from the second into the first.

$$V_i = \left[1 + \frac{R_1}{R_2} + sR_1C_1 \right] \left[1 + sR_2C_2 \right] V_o - \frac{R_1}{R_2} V_o$$

$$V_i = \left[1 + \frac{R_1}{R_2} + sR_1C_1 \right] \left[1 + sR_2C_2 \right] V_o - \frac{R_1}{R_2} V_o$$

6. Expand the product.

$$V_i = \left[1 + \cancel{\frac{R_1}{R_2}} + sR_1C_1 + sR_2C_2 + sR_1C_2 + s^2R_1R_2C_1C_2 \right] V_o - \cancel{\frac{R_1}{R_2}} V_o$$

7. Note that there are two terms that cancel – this always happens. Collect together similar powers and divide as needed to make a transfer function.

$$T(s) = \frac{V_o}{V_i} = \frac{1}{1 + (R_1C_1 + R_2C_2 + R_1C_2)s + s^2R_1R_2C_1C_2}$$


8. Finally, re-arrange to put it into standard form:

$$T(s) = \frac{\frac{1}{R_1R_2C_1C_2}}{s^2 + \left(\frac{1}{R_1C_1} + \frac{1}{R_2C_2} + \frac{1}{R_2C_1} \right) s + \frac{1}{R_1R_2C_1C_2}} = \frac{G_o\omega_o^2}{s^2 + \frac{\omega_o}{Q_P}s + \omega_o^2}$$

$$\omega_o^2 = \frac{1}{R_1R_2C_1C_2} \quad \frac{\omega_o}{Q_P} = \frac{1}{R_1C_1} + \frac{1}{R_2C_2} + \frac{1}{R_2C_1} \quad G_o = 1$$

Mesh current.

1. Write KVL equations around each loop.

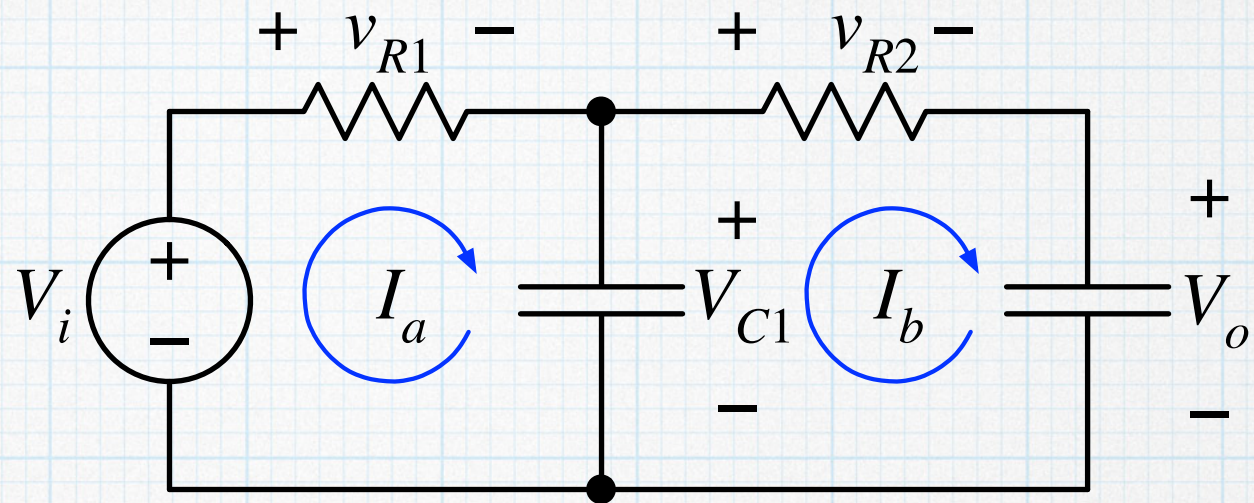

$$V_i - V_{R1} - V_{C1} = 0$$

$$V_{C1} - V_{R2} - V_{C2} = 0$$

$$V_o = I_b Z_{C2} = \frac{I_b}{sC_2}$$

2. Write in terms of the mesh currents and the impedances.

$$V_i - I_a Z_{R1} - (I_a - I_b) Z_{C1} = 0$$

$$(I_a - I_b) Z_{C1} - I_b Z_{R2} - I_b Z_{C2} = 0$$

3. Insert R 's and C 's.

$$V_i - I_a R_1 - \frac{I_a - I_b}{sC_1} = 0$$

$$\frac{I_a - I_b}{sC_1} - I_b R_2 - \frac{I_b}{sC_2} = 0$$

4. Rearrange.

$$I_a \left(R_1 + \frac{1}{sC_1} \right) - \frac{I_b}{sC_1} = V_i$$

$$-I_a + I_b \left(1 + \frac{C_1}{C_2} + sR_2 C_1 \right) = 0$$

5. Eliminate I_a . (Solve second equation of step 4 for I_a and substitute.)

$$I_b \left(1 + \frac{C_1}{C_2} + sR_2C_1 \right) \left(R_1 + \frac{1}{sC_1} \right) I_b - \frac{I_b}{sC_1} = V_i$$

6. Expand the product. Note that two terms cancel.

$$I_b \left(R_1 + \frac{R_1C_1}{C_2} + sR_1R_2C_1 + \cancel{\frac{1}{sC_1}} + \frac{1}{sC_2} + R_2 - \cancel{\frac{1}{sC_1}} \right) = V_i$$

7. Substitute sC_2V_o for I_b .

$$sC_2V_o \left(R_1 + \frac{R_1C_1}{C_2} + sR_1R_2C_1 + \frac{1}{sC_2} + R_1 \right) = V_i$$

8. Multiply through by sC_2 . Re-arrange to form a transfer function

$$T(s) = \frac{V_o}{V_i} = \frac{1}{sC_2R_1 + sR_1C_1 + s^2R_1R_2C_1C_2 + 1 + sR_1C_2}$$



9. Re-cast into standard form. Same as the node-voltage result.

$$T(s) = \frac{\frac{1}{R_1R_2C_1C_2}}{s^2 + \left(\frac{1}{R_1C_1} + \frac{1}{R_2C_2} + \frac{1}{R_2C_1} \right) s + \frac{1}{R_1R_2C_1C_2}}$$

Two voltage dividers

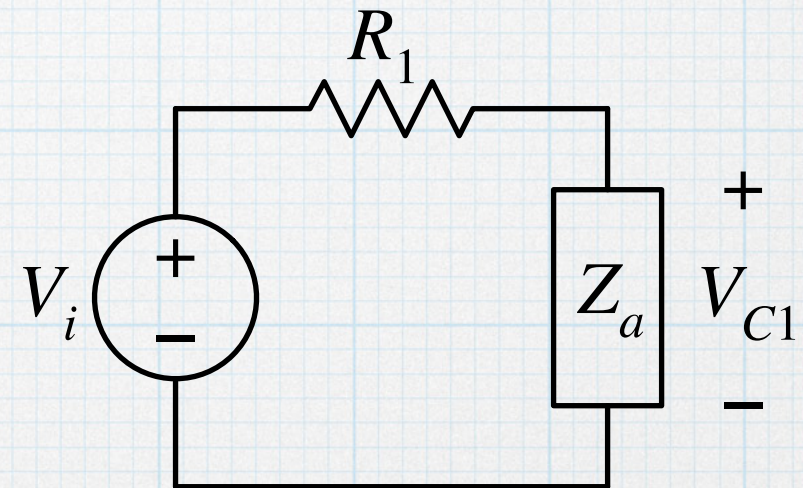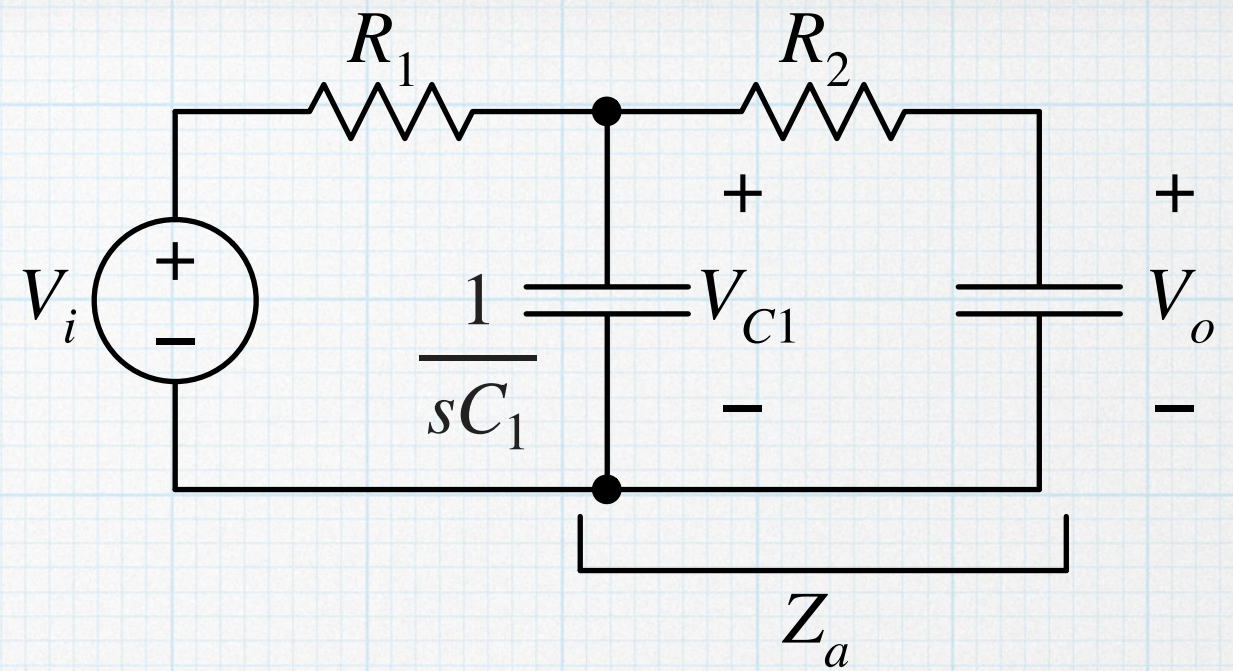1. Combine Z_{C1} , Z_{R2} , and Z_{C2} in order to find V_{C1} .

$$\begin{aligned} Z_a &= Z_{C1} \parallel (Z_{R2} + Z_{C2}) \\ &= \left(\frac{1}{sC_1} \right) \parallel \left(R_2 + \frac{1}{sC_2} \right) \\ &= \frac{\frac{1}{sC_1} \left(R_2 + \frac{1}{sC_2} \right)}{\frac{1}{sC_1} + R_2 + \frac{1}{sC_2}} \end{aligned}$$



2. Do the first voltage divider to find V_{C1} .

$$V_{C1} = \frac{Z_a}{Z_a + Z_{R1}} V_i = \frac{\frac{\frac{1}{sC_1} \left(R_2 + \frac{1}{sC_2} \right)}{\frac{1}{sC_1} + R_2 + \frac{1}{sC_2}}}{\frac{\frac{1}{sC_1} \left(R_2 + \frac{1}{sC_2} \right)}{\frac{1}{sC_1} + R_2 + \frac{1}{sC_2}} + R_1} V_i$$

3. Simplify!

$$V_{C1} = \frac{\frac{1}{sC_1} \left(R_2 + \frac{1}{sC_2} \right)}{\frac{1}{sC_1} \left(R_2 + \frac{1}{sC_2} \right) + R_1 \left(\frac{1}{sC_1} + R_2 + \frac{1}{sC_2} \right)} V_i$$

4. Simplify some more!!

$$V_{C1} = \frac{(1 + sR_2C_2)}{1 + sR_2C_2 + sR_1C_1 + sR_1C_2 + s^2R_1R_2C_1C_2} V_i$$

5. The second voltage divider gives V_o in terms of V_{C1} .

$$V_o = \frac{Z_{C2}}{Z_{C2} + Z_{R2}} V_{C2} = \frac{\frac{1}{sC_2}}{\frac{1}{sC_2} + R_2} V_{C2} = \frac{1}{1 + sR_2C_2} V_{C2}$$

6. Put the two together. Note the convenient cancellation top and bottom.

$$V_o = \left[\frac{1}{1 + sR_2C_2} \right] \left[\frac{(1 + sR_2C_2)}{1 + sR_2C_2 + sR_1C_1 + sR_1C_2 + s^2R_1R_2C_1C_2} V_i \right]$$

7. Finally, we have the transfer function:


$$T(s) = \frac{V_o}{V_i} = \frac{1}{1 + sR_2C_2 + sR_1C_1 + sR_1C_2 + s^2R_1R_2C_1C_2}$$

8. Put it in standard form.

$$T(s) = \frac{\frac{1}{R_1R_2C_1C_2}}{s^2 + \left(\frac{1}{R_1C_1} + \frac{1}{R_2C_2} + \frac{1}{R_2C_1} \right) s + \frac{1}{R_1R_2C_1C_2}} \quad \text{Same.}$$

A buffer makes the math easier

All of the math seems a bit unfair, given that the ladder circuits are essentially combinations of simple first-order circuits. Of course the problem is that the two first-order circuits affect each other once they are connected — they cannot be treated independently. However, if we could keep the two first-order circuits separate in some fashion, then we could simply multiply the first-order functions to obtain the second-order function. Of course, this is exactly what buffer amps were made for. Consider the circuit below.

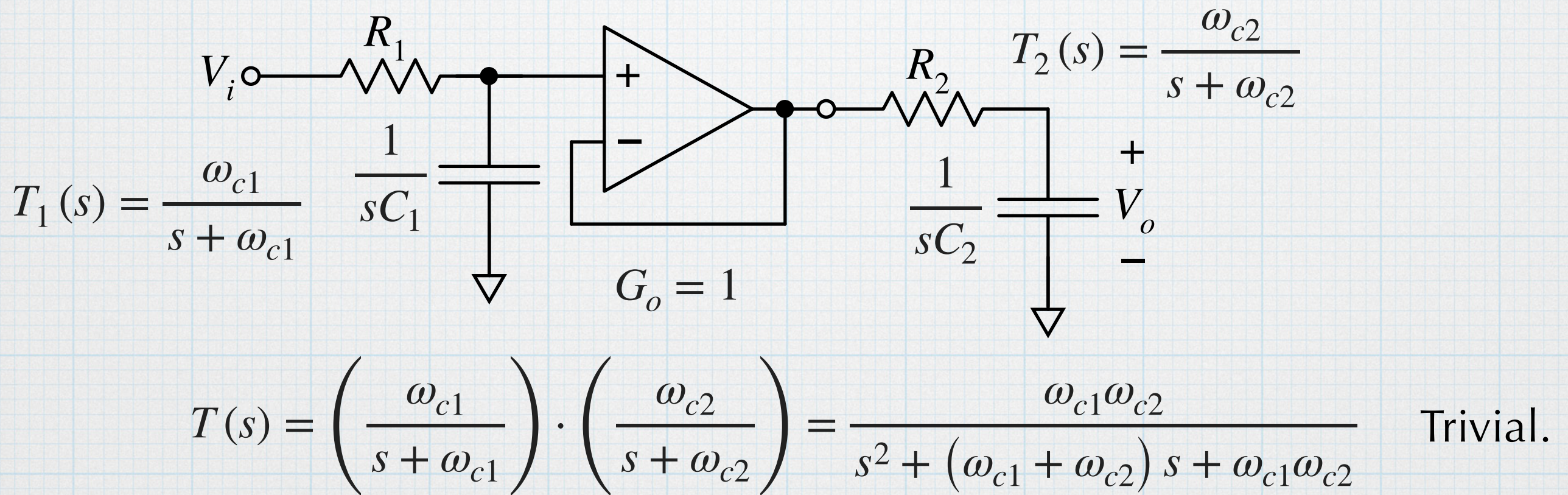

Of course, the price for simpler math is the need for an amp and supplies.